

# Solutions to Exercises

## Chapter 1

**Exercise 1.** Use Eq. (1.6) and take the resistivity value from Table 1.2. Also, the wire has diameter  $1 \text{ mm} = 10^{-3} \text{ m}$  so the area is  $A = \pi r^2 = \pi(\frac{10^{-3}}{2} \text{ m})^2 = 7.85 \times 10^{-3} \text{ m}^2$ . Finally, the length of the wire is  $1 \text{ m}$ , so  $R = \rho \frac{L}{A} = (100 \times 10^{-8} \Omega \cdot \text{m})(\frac{1 \text{ m}}{7.85 \times 10^{-3} \text{ m}^2}) = 1.27 \Omega$ .

**Exercise 2.** Equation (1.7) gives  $P = I^2 R$  for resistors. Thus  $I_{max} = \sqrt{(P/R)}$ . For the  $10 \text{ W}$  resistor we obtain  $I_{max} = \sqrt{(10 \text{ W}/10 \text{ k}\Omega)} = 0.032 \text{ A}$  and for the quarter-watt resistor  $I_{max} = \sqrt{(0.25 \text{ W}/10 \text{ k}\Omega)} = 0.005 \text{ A}$ .

**Exercise 3.** Equation (1.8) gives  $P = V^2/R$  for resistors. For the  $100 \Omega$  resistor we obtain  $P = (100 \text{ V})^2/100 \Omega = 100 \text{ W}$  while for the  $100 \text{ k}\Omega$  resistor we obtain  $P = (100 \text{ V})^2/100 \text{ k}\Omega = 0.1 \text{ W}$ .

**Exercise 4.** The current through  $R_3$  is the same as the current supplied by the battery. To find this current, we first find the total resistance of the circuit. The parallel combination of  $R_1$  and  $R_2$  is  $\frac{R_1 R_2}{R_1 + R_2} = \frac{6 \cdot 5}{6 + 5} = 2.73 \Omega$ . This resistance is then in series with  $R_3$  so  $R_{tot} = 3 \Omega + 2.73 \Omega = 5.73 \Omega$  and  $I_3 = V_1/R_{tot} = 5 \text{ V}/5.73 \Omega = 0.873 \text{ A}$ .

**Exercise 5.** Building on the result of the previous problem, the voltage across  $R_1$  and  $R_2$  is  $V_1 - I_3 R_3 = 5 \text{ V} - (0.873 \text{ A})(3 \Omega) = 2.38 \text{ V}$ . Therefore,  $I_2 = (2.38 \text{ V})/(6 \Omega) = 0.397 \text{ A}$  and  $I_1 = (2.38 \text{ V})/(5 \Omega) = 0.476 \text{ A}$ .

**Exercise 6.** When the meter is connected, the input resistance of the meter  $R_m$  will be in parallel with the  $1 \text{ k}\Omega$  resistor (call this resistor  $R_2$ ). The resulting circuit will still be a voltage divider, but  $R_2$  is replaced by the parallel combination of  $R_2$  and  $R_m$ ,  $R_2//R_m = \frac{R_2 R_m}{R_2 + R_m}$ . The voltage across this resistance is then given by the voltage divider equation [Eq. (1.21)]:

$$V_{out} = V_{in} \frac{R_2//R_m}{R_1 + (R_2//R_m)} = V_{in} \frac{R_2 R_m}{R_1 R_2 + R_1 R_m + R_2 R_m}$$

where we have called the  $2 \text{ k}\Omega$  resistor  $R_1$ . Putting in the numbers:


$$R_m = 100 \Omega : \quad V_{out} = 3 \text{ V} \frac{(1 \text{ k}\Omega)(100 \Omega)}{(2 \text{ k}\Omega)(1 \text{ k}\Omega) + (2 \text{ k}\Omega)(100 \Omega) + (1 \text{ k}\Omega)(100 \Omega)} = 0.130 \text{ V}$$

$$R_m = 1 \text{ k}\Omega : \quad V_{out} = 3 \text{ V} \frac{(1 \text{ k}\Omega)(1 \text{ k}\Omega)}{(2 \text{ k}\Omega)(1 \text{ k}\Omega) + (2 \text{ k}\Omega)(1 \text{ k}\Omega) + (1 \text{ k}\Omega)(1 \text{ k}\Omega)} = 0.600 \text{ V}$$

$$R_m = 50 \text{ k}\Omega : V_{\text{out}} = 3 \text{ V} \frac{(1 \text{ k}\Omega)(50 \text{ k}\Omega)}{(2 \text{ k}\Omega)(1 \text{ k}\Omega) + (2 \text{ k}\Omega)(50 \text{ k}\Omega) + (1 \text{ k}\Omega)(50 \text{ k}\Omega)} = 0.987 \text{ V}$$

$$R_m = 1 \text{ M}\Omega : V_{\text{out}} = 3 \text{ V} \frac{(1 \text{ k}\Omega)(1 \text{ M}\Omega)}{(2 \text{ k}\Omega)(1 \text{ k}\Omega) + (2 \text{ k}\Omega)(1 \text{ M}\Omega) + (1 \text{ k}\Omega)(1 \text{ M}\Omega)} = 0.999 \text{ V}$$

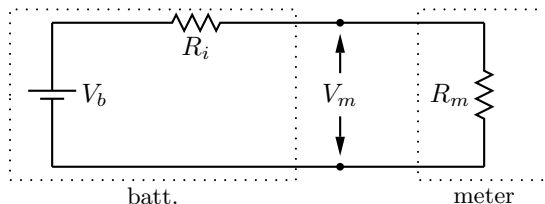**Exercise 7.** When the voltmeter is attached the circuit appears as shown below.




This is a voltage divider so  $V_m = V_b \frac{R_m}{R_i + R_m}$ . Solving for  $R_i$  gives  $R_i = R_m \frac{V_b}{V_m} - R_m = (1000 \Omega) \frac{1.5 \text{ V}}{0.9 \text{ V}} - 1000 \Omega = 667 \Omega$ .

**Exercise 8.** Referring to the diagram for Exercise 7, we have  $V_m = V_b \frac{R_m}{R_m + R_i} = (1.5 \text{ V}) \frac{1 \text{ M}\Omega}{1 \text{ M}\Omega + 667 \Omega} = 1.499 \text{ V}$ .

**Exercise 9.** Start by combining the  $10 \Omega$  and  $5 \Omega$  resistors in series to form a  $15 \Omega$  resistor. This, in parallel with the existing  $15 \Omega$  resistor gives a  $7.5 \Omega$  resistor. This resistor is in series with the  $3 \Omega$  and  $2 \Omega$ , giving a total of  $3 + 7.5 + 2 = 12.5 \Omega$  across the terminals.

**Exercise 10.** From the result of Exercise 9 we know that the current supplied by the battery is  $I_1 = V_{\text{bat}}/R_{\text{tot}} = 25 \text{ V}/12.5 \Omega = 2 \text{ A}$ . This means the voltage across the  $15 \Omega$  resistor is  $V_{15} = 25 \text{ V} - I_1(3 \Omega + 2 \Omega) = 15 \text{ V}$ . This is also the voltage across the series combination of the  $10 \Omega$  and  $5 \Omega$  resistors. Thus the current through the  $10 \Omega$  resistor is  $V_{15}/(10 \Omega + 5 \Omega) = 1 \text{ A}$ .

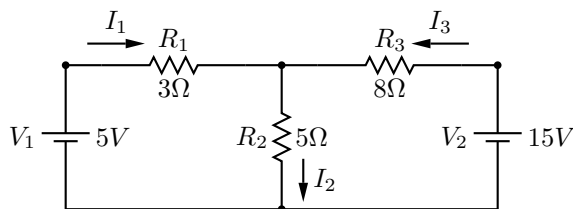**Exercise 11.** Assign current names and directions as shown below. For the left and right



halves of the circuit, KVL gives

$$\text{a) } V_1 - I_1 R_1 - I_2 R_2 = 0$$

$$\text{b) } V_2 - I_3 R_3 - I_2 R_2 = 0 \rightarrow I_3 = \frac{V_2 - I_2 R_2}{R_3}$$

and KCL gives  $I_1 + I_3 = I_2$  or  $I_1 = I_2 - I_3$ . Using this last result in a) gives

$$V_1 - (I_2 - I_3)R_1 - I_2 R_2 = 0$$