

$$\underline{2.1} \quad V = \sqrt{2} \times 120 \cos(\omega t + 30^\circ) \Rightarrow V = 120 \angle 30^\circ \quad V$$

$$i = \sqrt{2} \times 10 \cos(\omega t - 30^\circ) \Rightarrow I = 10 \angle -30^\circ \quad A$$

$$(a) \quad P(t) = |V||I| [\cos \phi + \cos(2\omega t + \angle V + \angle I)] \\ = 600 + 1200 \cos 2\omega t \quad W$$

$$S = VI^* = 1200 \angle 60^\circ = P + jQ \Rightarrow P = 600 \text{ W}, Q = 1039 \text{ VAR}$$

$$(b) \quad Z = V/I = 12 \angle 60^\circ = 6 + j10.39 = R + jX \Rightarrow R = 6, X = 10.39$$

2.2 (a) Using (2.3) we find  $P_{max} = 1707 = |V||I|(\cos \phi + 1)$   
 and  $P_{min} = -293 = |V||I|(\cos \phi - 1)$ . Then, since  $|V| = 100$ , we  
 get  $|I| = 10$  and  $\cos \phi = \pm 45^\circ$ . Pick  $\phi = 45^\circ \Rightarrow Z = 10 \angle 45^\circ =$   
 $7.07 + j7.07 = R + jX \Rightarrow R = 7.07, X = 7.07$

$$(b) \quad S = VI^* = Z|I|^2 = (7.07 + j7.07) 10^2 \Rightarrow P = 707, Q = 707$$

(c) For simplicity assume  $i(t) = \sqrt{2}/|I| \cos \omega t$ . Then

$$P_L(t) = V_L(t)i(t) = L \frac{di}{dt} = -2\omega L|I|^2 \cos \omega t \sin \omega t = -\omega L|I|^2 \sin 2\omega t$$

$$P_{Lmax} = \omega L|I|^2 = 707 = Q. \text{ Thus } P_{Lmax} = Q. \text{ The same!}$$

$$\underline{2.3} \quad 0.7 \text{ PF lagging} \Rightarrow \phi = 45.57^\circ, Q = 5.10 \text{ MVAR}$$

0.9 PF lagging  $\Rightarrow \phi = 25.84^\circ, Q = 2.42 \text{ MVAR}$ . Capacitor must supply  $5.10 - 2.42 = 2.68 \text{ MVAR}$ .

$$\underline{2.4} \quad 0.707 \text{ PF lagging} \Rightarrow S_{3\phi} = 200 + j200 \text{ kVA}. \text{ Cap supplies } 50 \text{ kVAR. Resultant } S_{3\phi} = 200 + j150 \text{ kVA} \Rightarrow \text{PF} = 0.80.$$

$$|S| = \frac{|S_{3\phi}|}{3} = \frac{250 \times 10^3}{3} = |V||I| = \frac{440}{\sqrt{2}}|I| \Rightarrow |I| = 329 \text{ A}$$

$$\underline{2.5} \quad 0.9 \text{ PF lagging} \Rightarrow \phi = 25.84^\circ$$


$$(a) \quad S = 10 + j4.84 \text{ kVA}$$

$$(b) \quad 10 \times 10^3 = 416 \times |I| \times 0.9 \Rightarrow |I| = 26.71 \text{ A}$$

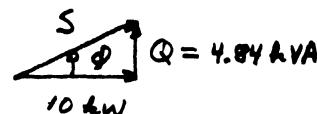(c) Using (2.3), (or first principles) we get

$$P(t) = 10 \times 10^3 + 11.11 \times 10^3 \cos(2\omega t + 25.84^\circ)$$

Note: The average value of  $P(t)$  is  $10 \text{ kW}$



2.6 Because system is balanced  $V_{ab} = 208 \angle 120^\circ$ ,  $V_{bc} = 208 \angle 0^\circ$ .  
 Using (2.17) or Fig 2.11,  $V_{an} = 120 \angle 90^\circ \Rightarrow V_{bn} = 120 \angle -30^\circ$ ,  
 $V_{cn} = 120 \angle -150^\circ$ . Using per phase analysis,  $I_a = 12 \angle 105^\circ \Rightarrow$   
 $I_b = 12 \angle -15^\circ$ ,  $I_c = 12 \angle -135^\circ$ .

$$\underline{2.7} \quad S = V I^* = V(YV)^* = Y^* N V^2 = Y_C^* + Y_L^* + Y_R^*$$

$$= -j5 + j10 + 0.1 = 0.1 + j5$$

2.8 (a) Using loop or nodal analysis we find, after much work,  
 $I_a = 0.9123 \angle -90.351^\circ$ ,  $I_b = 0.9123 \angle -209.65^\circ$ ,  $I_c = 0.9929 \angle 30^\circ$

(b) Using per phase analysis  $I_a = 1 \angle 0^\circ / j 1.1 = 0.9091 \angle -90^\circ$ ,  
 then,  $I_b = 0.9091 \angle -210^\circ$ ,  $I_c = 0.9091 \angle 30^\circ$ .

2.9 Proceeding by analogy with  $3\phi$ , we note


$$E_{ab} = E_{an} - E_{bn} = E_{an} \left(1 - e^{-j\pi/2}\right) = \sqrt{2} E_{an} e^{j\pi/4}.$$

Thus  $E_{an} = \frac{1}{\sqrt{2}} E_{ab} e^{-j\pi/4}$ , and  $E_{an}, E_{bn}, E_{cn}, E_{dn}$  form a pos. seq. set of  $4\phi$  voltages. Doing per phase (phase) analysis we have

$$\frac{1}{\sqrt{2}} \angle 45^\circ \left( \begin{array}{c} + \\ - \end{array} \right) j1 \left( \begin{array}{c} + \\ - \end{array} \right) -j0.5 \Rightarrow I_a = \frac{\frac{1}{\sqrt{2}} \angle -45^\circ}{j0.5} = \sqrt{2} \angle -135^\circ$$

$$\text{Then } I_b = \sqrt{2} \angle -225^\circ, \quad I_c = \sqrt{2} \angle -315^\circ, \quad I_d = \sqrt{2} \angle -405^\circ$$

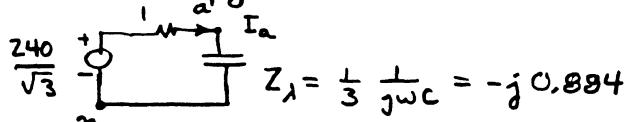2.10 Using per phase circuit we find  $I_a = 103.8 \angle 41.5^\circ$ .



$$\text{Then } |I_4| = 103.8 \text{ A}$$


$$V_{a'1n} = Z_A I_a = 91.76 \angle -48.5^\circ \Rightarrow |V_{a'b'}| = \sqrt{3} \cdot 91.76 = 158.9 \text{ V}$$

$$S_{load} = V_{a'x} I_a^* = 9524 \angle -90^\circ$$

$$S_{\text{load}}^{3\phi} = 3 S_{\text{load}} = 28574 \angle -90^\circ \text{ W}$$

2.11 Assume pos. seg. operation.  $V_{a''b''} = V_{a''n} - V_{b''n} = \sqrt{3} V_{a''n} e^{j\pi/6} \Rightarrow V_{a''n} = \frac{1}{\sqrt{3}} V_{a''b''} e^{-j\pi/6} = \frac{1}{\sqrt{3}} \angle -30^\circ$

Per Phase Clt

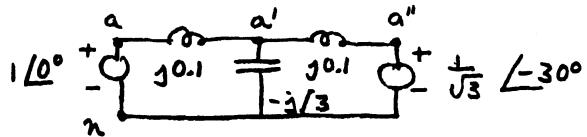


Using superposition & voltage divider law we get

$$V_{a'n} = 0.899 \angle -10.89^\circ \Rightarrow V_{b'n} = 0.899 \angle -130.89^\circ \text{ and}$$

$$V_{c'n} = 0.899 \angle -250.89^\circ. \text{ Then } V_{a'b'} = 1.557 \angle 19.11^\circ$$

2.12 Assume pos. seg..

Per Phase Clt

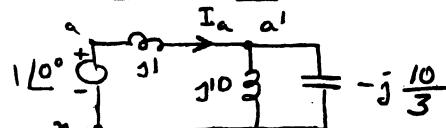

Combining parallel elements we have  $Z_{ll} = -j5$ .  $I_a = 0.25 \angle 90^\circ$

$$V_{a'n} = -j5 \cdot j0.25 = 1.25 \angle 0^\circ$$

$$V_{a'b'} = 2.165 \angle 30^\circ \Rightarrow I_{cap} = 2.165 \angle 120^\circ$$

$$S_{load} = 3 V_{a'n} I_a = 0.3125 \angle -90^\circ$$

2.13

$$(a) V_{bc} = 208 \angle -120^\circ, V_{ca} = 208 \angle 120^\circ$$

$$V_{an} = \frac{208}{\sqrt{3}} \angle -30^\circ \Rightarrow I_a = 1.20 \angle -90^\circ$$


$$\text{then } I_b = 1.20 \angle -210^\circ, I_c = 1.20 \angle -330^\circ$$

$$(b) V_{bc} = 208 \angle 120^\circ, V_{ca} = 208 \angle -120^\circ$$


$$V_{an} = \frac{208}{\sqrt{3}} \angle 30^\circ \Rightarrow I_a = 1.20 \angle -30^\circ$$

$$I_b = 1.20 \angle 90^\circ, I_c = 1.20 \angle -150^\circ$$

2.14 Per Phase Clt. Problem reduces to picking  $Z$  so that  $|V_{a'n}| > |V_{an}|$ . It helps to draw some phasor diagrams.

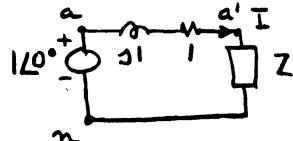

I.  $Z = j\omega L$

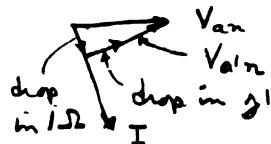

$$\text{Clearly } |V_{a'n}| < |V_{an}|$$

II.  $Z = R$



$$\text{Clearly } |V_{a'n}| < |V_{an}|$$

III.  $Z = -j\frac{1}{\omega C}$

For example  $Z = -j2$

$$I = \frac{1}{\sqrt{2}} \angle 45^\circ$$

$$V_{a'n} = \sqrt{2} \angle -45^\circ$$

$|V_{a'n}| > |V_{an}|$   
This is O.K.


2.15 Since  $E_a + E_b + E_c = 0$ , neutrals are at same potential.

$Z = E_a / I_a = \sqrt{2} \angle 55^\circ$ . For each  $Z$ ,  $S = VI^* = |V|^2 / Z^*$ . Thus

$$S^{3\phi} = \frac{(\sqrt{2})^2 + 1^2 + 1^2}{\sqrt{2} \angle -55^\circ} = 2\sqrt{2} \angle 55^\circ.$$


---

3.1

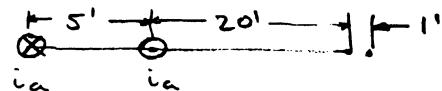

$$\frac{\mu_0}{2\pi} = 2 \times 10^{-7}, |I_a| = 100$$


(Upward) flux linkages of telephone wires

$$\lambda = 2 \times 10^{-7} \left[ i_a \ln \frac{26}{25} - i_a \ln \frac{21}{20} \right] = -0.00957 \times 2 \times 10^{-7} i_a$$

$$V_{tel} = \frac{d\lambda}{dt} \Rightarrow V_{tel} = j\omega \times (-0.00957 \times 2 \times 10^{-7}) \times 100 \text{ V/meter}$$

Since 1 mile = 1.609 km,  $|V_{tel}| = 0.116 \text{ V/mile}$


3.2

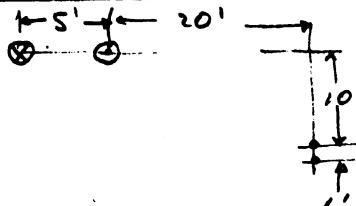

$$\begin{aligned} \lambda &= 2 \times 10^{-7} i_a \left[ \ln \frac{\sqrt{25^2 + 11^2}}{\sqrt{25^2 + 10^2}} - \ln \frac{\sqrt{20^2 + 11^2}}{\sqrt{20^2 + 10^2}} \right] \\ &= -0.066294 \times 2 \times 10^{-7} i_a \\ \Rightarrow |V_{tel}| &= 0.076 \text{ V/mile} \end{aligned}$$


---

3.3

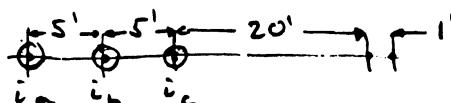

$$\lambda = 2 \times 10^{-7} \left[ i_a \ln \frac{31}{30} + i_b \ln \frac{26}{25} + i_c \ln \frac{21}{20} \right]$$

$$= 2 \times 10^{-7} [0.0328 i_a + 0.0392 i_b + 0.0488 i_c]$$

$$V_{tel} = j\omega \times 2 \times 10^{-7} [0.0328 I_a + 0.0392 I_b + 0.0488 I_c]$$

$$|V_{tel}| = 377 \times 2 \times 10^{-7} \times 100 \times |0.0328 + 0.0392 \angle -120^\circ + 0.0488 \angle 120^\circ|$$


$$= 1048 \times 10^{-7} \text{ V/meter} = 0.1692 \text{ V/mile}$$


---

3.4 The telephone wires are transposed every 1000 ft.

Cancellation occurs in all but 720' of line  $\Rightarrow 0.0158 \text{ V}$ .

3.5

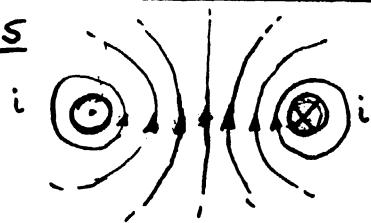

The flux linkages due to the current in the left conductor is  $\approx$

$$\lambda_1 = \frac{\mu_0}{2\pi} i \left[ \frac{M_r}{4} + \ln \frac{D}{r} \right] = i \frac{\mu_0}{2\pi} \ln \frac{D}{r}$$

Here we are neglecting partial flux linkages of the far (right) conductor. The current in the right conductor contributes an equal number of flux linkages. Thus (at least approximately),

$$l = 2\lambda_1 / i = \frac{\mu_0}{\pi} \ln \frac{D}{r} = 4 \times 10^{-7} \ln \frac{D}{r} \text{ H/meter}$$

3.6 If each conductor is hollow then there are no partial flux linkages and in (3.13) the term involving  $M_r$  is absent. Then  $r' = r$  and

$$l = \frac{\mu_0}{2\pi} \ln \frac{D}{r} \text{ H/m}$$

3.7 The hint is misleading. A better hint for combining the 7 (unequal) inductances  $l_1, l_2, \dots, l_7$  would be to use the average inductance i.e. let  
 $l_a = \frac{l_{av}}{7} = \frac{l_1 + l_2 + \dots + l_7}{7^2}$  Returning to the problem, parallelizing the steps which lead to (3.27) we have

$$\begin{aligned} \lambda_1 &= \frac{\mu_0}{2\pi} \left[ \frac{l_a}{7} \left( \ln \frac{1}{d_{11}} + \ln \frac{1}{d_{12}} + \dots + \ln \frac{1}{d_{17}} \right) \right. \\ &\quad + \frac{i_b}{7} \left( \ln \frac{1}{d_{18}} + \ln \frac{1}{d_{19}} + \dots + \ln \frac{1}{d_{1,21}} \right) \\ &\quad \left. + \frac{i_c}{7} \left( \ln \frac{1}{d_{1,15}} + \ln \frac{1}{d_{1,16}} + \dots + \ln \frac{1}{d_{1,21}} \right) \right] \\ &\approx \frac{\mu_0}{2\pi} l_a \ln \frac{D}{(d_{11} \dots d_{17})^{1/7}} \Rightarrow l_1 = 7 \times \frac{\mu_0}{2\pi} \ln \frac{D}{(d_{11} \dots d_{17})^{1/7}} \end{aligned}$$